

Electronics Post

[HOME](#) [MCQ](#) [SOLVED PROBLEMS](#) [TUTORIALS](#) » [QUESTIONS](#) » [ABOUT](#) [CONTACT US](#)



Solved Problems on Transistor Biasing

BASIC ELECTRONICS SOLVED PROBLEMS BY SASMITA JANUARY 9, 2020

Q1. An npn silicon transistor has $V_{CC} = 6\text{ V}$ and the collector load $R_C = 2.5\text{ k}\Omega$. Find : (i) The maximum collector current that can be allowed during the application of signal for faithful amplification. (ii) The minimum zero signal collector current required.

Solution :



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

PCBWay **Only \$30**

- Free shipping
- Free stencil

PCB Assembly Service

- Component sourcing
- Quality assurance


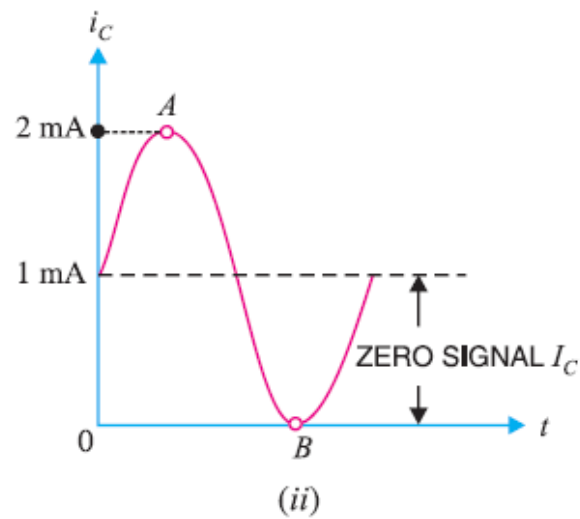



Fig.1

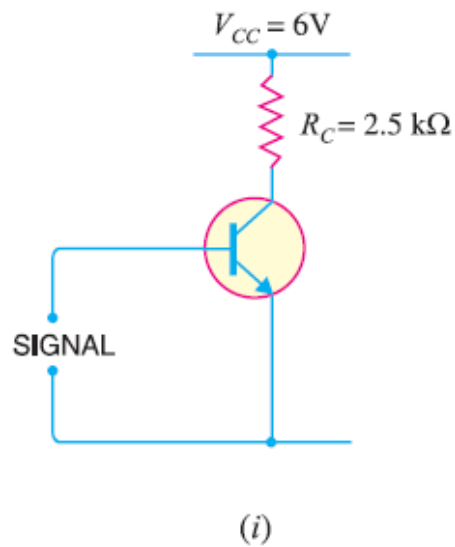

MV vacuum circuit breaker

VCB manufacturer

Buy high quality medium voltage vacuum circuit breaker in bulk from trusted supplier.

jggyelectrical.com

OPEN


HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

silicon transistor.

∴ Max. voltage allowed across RC = 6 – 1 = 5 V

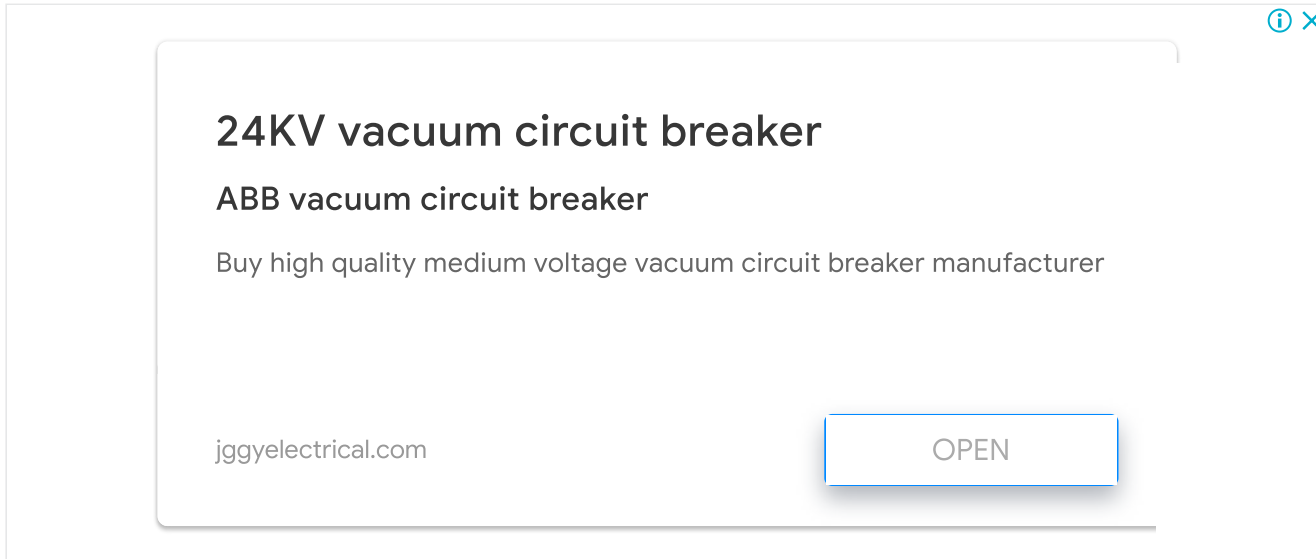∴ Max. allowed collector current = 5 V/RC = 5 V/2.5 kΩ = **2 mA**



24KV vacuum circuit breaker
ABB vacuum circuit breaker
 Buy high quality medium voltage vacuum circuit breaker manufacturer
 jggyelectrical.com
 OPEN

Thus, the maximum collector current allowed during any part of the signal is 2 mA. If the collector current is allowed to rise above this value, VCE will fall below 1 V. Consequently, value of β will fall, resulting in unfaithful amplification.

(ii) During the negative peak of the signal, collector current can at the most be allowed to become zero. As the negative and positive half cycles of the signal are

Find Out More

Box Elder Innovations

Understanding charge propagation insulating materials aids in material selection.

boxelderinnovations.com

OPEN

Categories

- Amplifier (10)
- Amplitude Modulation (18)
- Angle Modulation (3)
- Basic Electrical Engineering (1)
- Basic electronics Solved problems (8)
- Big Data (2)
- Blogging (1)
- Boolean Logic (2)
- Capacitors (2)

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

24KV vacuum circuit breaker

ABB vacuum circuit breaker

Buy high quality medium voltage vacuum circuit breaker manufacturer

jggyelectrical.com

OPEN

- Conversion Rate Optimization (2)
- Converters (1)
- CRO (5)
- DC-DC Converters (2)
- Diac (1)
- Differential Amplifier (1)
- Digital multiplexing (1)
- Electric Current and Ohm's Law (1)
- Electronics and Communication Engineering Questions and Answers (3)
- Electronics Instruments (1)
- Electronics Questions and Answers (20)
- Filter Circuits (9)
- Founder Speaks (3)
- GATE Questions and Answers (1)
- Integrated Circuits (7)
- Interview (8)
- Introduction to Electronics (1)
- JK Flip Flop (3)
- Logic circuits (1)
- Logic Gates and Boolean Algebra (10)
- Long Questions and Answers (3)

During the positive peak of the signal [point A in Fig. 1(ii)], $i_C = 1 + 1 = 2\text{mA}$

And during the negative peak (point B), $i_C = 1 - 1 = 0\text{ mA}$

Q2. A transistor employs a $4\text{ k}\Omega$ load and $V_{CC} = 13\text{V}$. What is the maximum input signal if $\beta = 100$? Given $V_{knee} = 1\text{V}$ and a change of 1V in V_{BE} causes a change of 5mA in collector current.

Solution :

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

∴ Max. allowed voltage across RC = $13 - 1 = 12 \text{ V}$

∴ Max. allowed collector current, $i_C = 12 \text{ V} / RC = 12 \text{ V} / 4 \text{ K}\Omega = 3 \text{ mA}$

Maximum base current, $i_B = i_C / \beta = 3 \text{ mA} / 100 = 30 \mu\text{A}$

Now Collector current / Base voltage (signal voltage) = 5 mA/V

∴ Base voltage (signal voltage) = Collector current / $(5 \text{ mA/V}) = 3 \text{ mA} / (5 \text{ mA/V}) =$
600 mV

Q3. Fig. 2 (i) shows biasing with base resistor method. (i) Determine the collector current I_C and collector-emitter voltage V_{CE} . Neglect small base-emitter voltage. Given that $\beta = 50$. (ii) If R_B in this circuit is changed to $50 \text{ k}\Omega$, find the new operating point.


Solution :

- Oscilloscopes (2)
- PCB (38)
- Popular (3)
- Product Reviews (1)
- Relay (2)
- Resistors (4)
- SCR (3)
- Semiconductor (6)
- Semiconductor Diode (7)
- Sequential Circuit (3)
- Short Questions (2)
- Short Questions and Answers (15)
- Signal Processing (3)
- Sinusoidal Oscillator (3)
- Special Purpose Diodes (1)
- Switching Circuits (2)
- Tech (16)
- Tech Advice (1)
- Tech News (2)
- Transistor (10)
- Triac (1)
- Uncategorized (11)




HV vacuum circuit breaker - 24KV vacuum
 circuit breaker

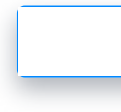
JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com



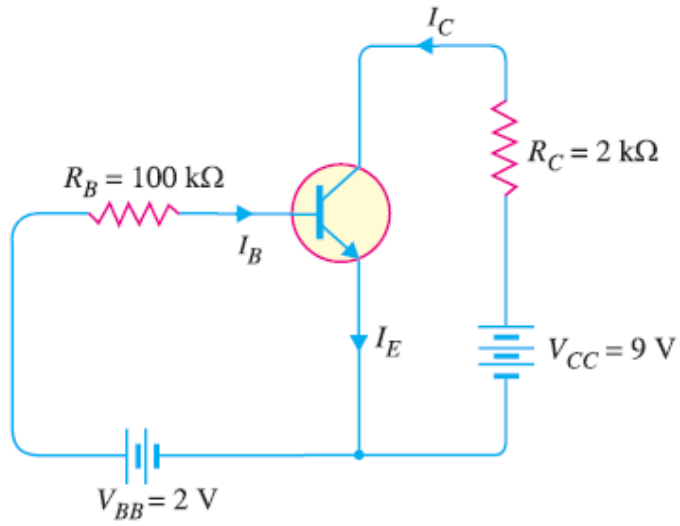- Waveform coding techniques (2)
- Zener Diode (1)



(i)

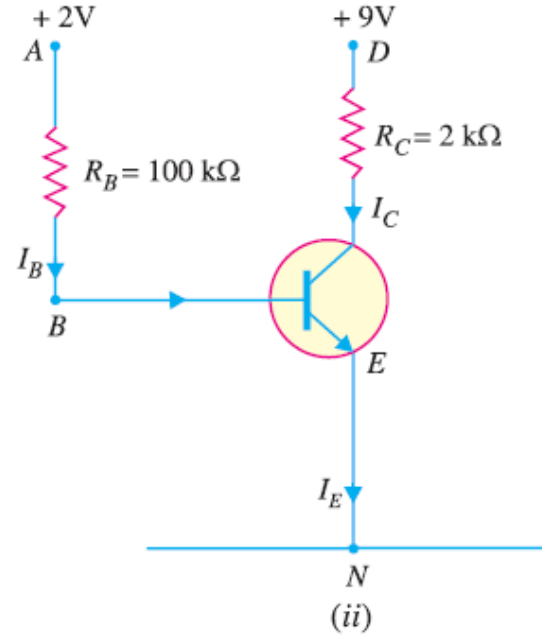

(ii)

24KV vacuum circuit breaker

ABB vacuum circuit breaker

Buy high quality medium voltage vacuum circuit breaker manufacturer

jggyelectrical.com

OPEN

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

In the circuit shown in Fig. 2 (i), biasing is provided by a battery V_{BB} ($= 2V$) in the base circuit which is separate from the battery V_{CC} ($= 9V$) used in the output circuit.

The same circuit is shown in a simplified way in Fig. 2 (ii). Here, we need show only the supply voltages, $+ 2V$ and $+9V$. It may be noted that negative terminals of the power supplies are grounded to get a complete path of current.

(i) Referring to Fig.2 (ii) and applying Kirchhoff 's voltage law to the circuit ABEN, we get,

$$I_B R_B + V_{BE} = 2V$$

As V_{BE} is negligible,

$$\therefore I_B = \frac{2V}{R_B} = \frac{2V}{100 \text{ k}\Omega} = 20 \mu\text{A}$$

$$\text{Collector current, } I_C = \beta I_B = 50 \times 20 \mu\text{A} = 1000 \mu\text{A} = \mathbf{1 \text{ mA}}$$

Applying Kirchhoff's voltage law to the circuit DEN, we get,

$$I_C R_C + V_{CE} = 9$$

$$\text{or } 1 \text{ mA} \times 2 \text{ k}\Omega + V_{CE} = 9$$

$$\text{or } V_{CE} = 9 - 2 = \mathbf{7V}$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com



$$\therefore \text{Collector current, } I_C = \beta I_B = 50 \times 40 = 2000 \mu\text{A} = 2 \text{ mA}$$

$$\text{Collector-emitter voltage, } V_{CE} = V_{CC} - I_C R_C = 9 - 2 \text{ mA} \times 2 \text{ k}\Omega = 5 \text{ V}$$

\therefore New operating point is **5 V, 2 mA**.

Q4. Fig. 3 (i) shows that a silicon transistor with $\beta = 100$ is biased by base resistor method. Draw the d.c. load line and determine the operating point. What is the stability factor ?

Solution :

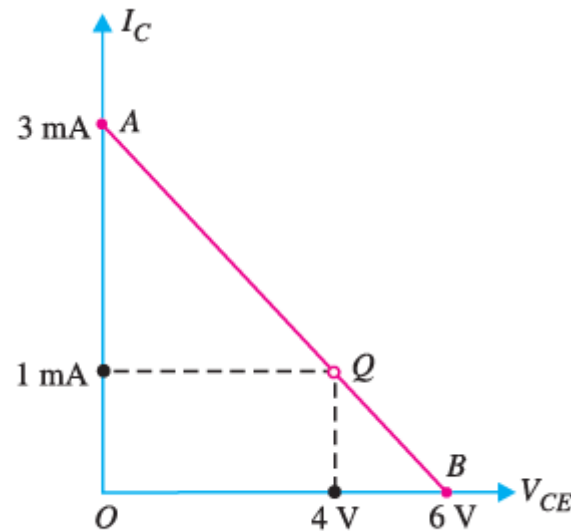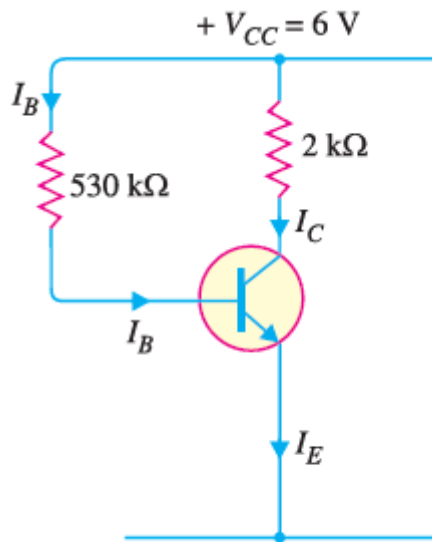

HV vacuum circuit breaker - 24KV vacuum
circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

D.C. load line

Referring to Fig. 3 (i), $V_{CE} = V_{CC} - I_C R_C$

When $I_C = 0$, $V_{CE} = V_{CC} = 6 \text{ V}$. This locates the first point B ($OB = 6\text{V}$) of the load line on collector-emitter voltage axis as shown in Fig. 3 (ii).

When $V_{CE} = 0$, $I_C = V_{CC}/R_C = 6\text{V}/2 \text{ k}\Omega = 3 \text{ mA}$.

This locates the second point A ($OA = 3\text{mA}$) of the load line on the collector current axis. By joining points A and B, d.c. load line AB is constructed as shown in Fig. 3(ii).

Operating point Q

As it is a silicon transistor, therefore, $V_{BE} = 0.7\text{V}$. Referring to Fig. 3(i), it is clear that :

$$I_B R_B + V_{BE} = V_{CC}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{(6 - 0.7) \text{ V}}{530 \text{ k}\Omega} = 10 \mu\text{A}$$

or
✓

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Fig. 3 (ii) shows the operating point Q on the d.c. load line. Its co-ordinates are $I_C = 1\text{mA}$ and $V_{CE} = 4\text{V}$.

$$\text{Stability factor} = \beta + 1 = 100 + 1 = 101$$

Q5. (i) A germanium transistor is to be operated at zero signal $I_C = 1\text{mA}$. If the collector supply $V_{CC} = 12\text{V}$, what is the value of R_B in the base resistor method? Take $\beta = 100$.

(ii) If another transistor of the same batch with $\beta = 50$ is used, what will be the new value of zero signal I_C for the same R_B ?

Solution :

$$\text{Given, } V_{CC} = 12\text{ V, } \beta = 100$$

As it is a Ge transistor, therefore, $V_{BE} = 0.3\text{ V}$

(i) Zero signal $I_C = 1\text{ mA}$

HV vacuum circuit breaker - 24KV vacuum
circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$\begin{aligned} \therefore \quad \text{Zero signal } I_B &= I_C/\beta = 1 \text{ mA}/100 = 0.01 \text{ mA} \\ \text{Using the relation, } V_{CC} &= I_B R_B + V_{BE} \\ \therefore \quad R_B &= \frac{V_{CC} - V_{BE}}{I_B} = \frac{12 - 0.3}{0.01 \text{ mA}} \\ &= 11.7 \text{ V}/0.01 \text{ mA} = \mathbf{1170 \text{ k}\Omega} \end{aligned}$$

(ii) Now $\beta = 50$

$$\begin{aligned} \text{Again using the relation, } V_{CC} &= I_B R_B + V_{BE} \\ \therefore \quad I_B &= \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 - 0.3}{1170 \text{ k}\Omega} \\ &= 11.7 \text{ V}/1170 \text{ k}\Omega = 0.01 \text{ mA} \\ \therefore \quad \text{Zero signal } I_C &= \beta I_B = 50 \times 0.01 = \mathbf{0.5 \text{ mA}} \end{aligned}$$

Q6. Calculate the values of three currents in the circuit shown in Fig. 4.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

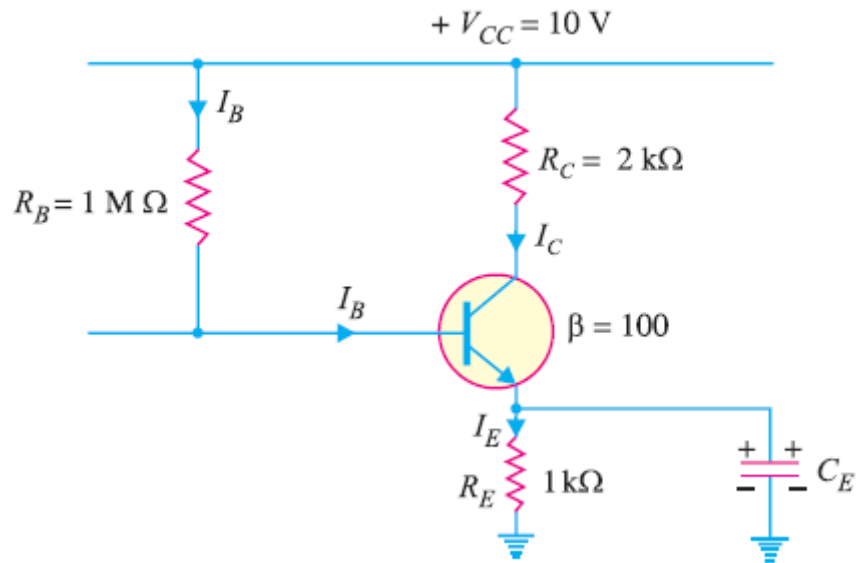


Fig. 4

Solution :

Applying Kirchhoff's voltage law to the base side and taking resistances in $\text{k}\Omega$ and currents in mA , we have,

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$V_{CC} = I_B R_B + V_{BE} + I_E \times 1$$

or $10 = 1000 I_B + 0 + (I_C + I_B)$

or $10 = 1000 I_B + (\beta I_B + I_B)$

or $10 = 1000 I_B + (100 I_B + I_B)$

or $10 = 1101 I_B$

$\therefore I_B = 10/1101 = 0.0091 \text{ mA}$

$I_C = \beta I_B = 100 \times 0.0091 = 0.91 \text{ mA}$

$I_E = I_C + I_B = 0.91 + 0.0091 = 0.919 \text{ mA}$

Q7. Design base resistor bias circuit for a CE amplifier such that operating point is $V_{CE} = 8\text{V}$ and $I_C = 2 \text{ mA}$. You are supplied with a fixed 15V d.c. supply and a silicon transistor with $\beta = 100$. Take base-emitter voltage $V_{BE} = 0.6\text{V}$. Calculate also the value of load resistance that would be employed

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

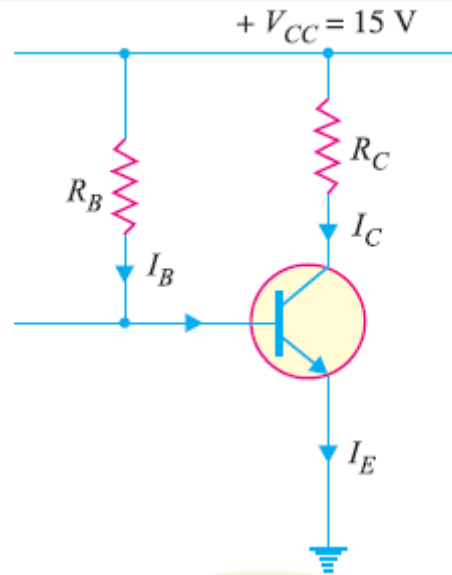


Fig. 5

$$V_{CC} = 15 \text{ V} ; \beta = 100 ; V_{BE} = 0.6 \text{ V}$$

$$V_{CE} = 8 \text{ V} ; I_C = 2 \text{ mA} ; R_C = ? ; R_B = ?$$

$$V_{CC} = V_{CE} + I_C R_C$$

or $15 \text{ V} = 8 \text{ V} + 2 \text{ mA} \times R_C$

$$\therefore R_C = \frac{(15 - 8) \text{ V}}{2 \text{ mA}} = 3.5 \text{ k}\Omega$$

$$I_B = I_C / \beta = 2 / 100 = 0.02 \text{ mA}$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Q8. A base bias circuit in Fig. 6 is subjected to an increase in temperature from 25°C to 75°C. If $\beta = 100$ at 25°C and 150 at 75°C, determine the percentage change in Q-point values (VCE and IC) over this temperature range. Neglect any change in VBE and the effects of any leakage current.

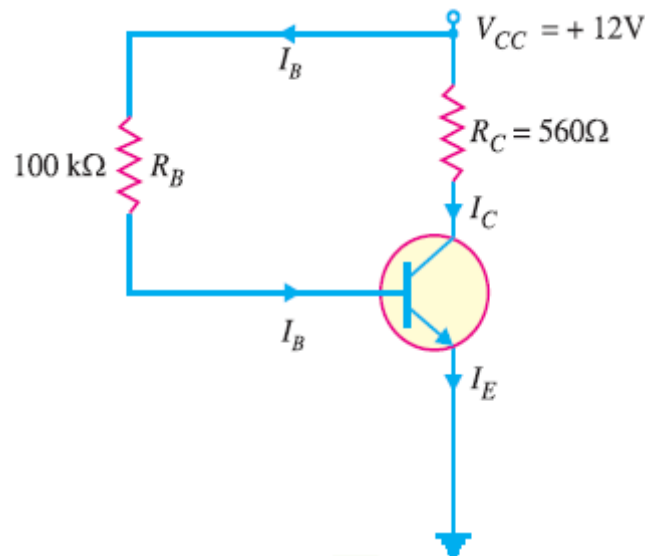


Fig 6

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$= \frac{12 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = 0.113 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 \times 0.113 \text{ mA} = 11.3 \text{ mA}$$

and $V_{CE} = V_{CC} - I_C R_C = 12 \text{ V} - (11.3 \text{ mA})(560 \Omega) = 5.67 \text{ V}$

At 75 °C :

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{100 \text{ k}\Omega} = 0.113 \text{ mA}$$

$$\therefore I_C = \beta I_B = 150 \times 0.113 \text{ mA} = 17 \text{ mA}$$

and $V_{CE} = V_{CC} - I_C R_C = 12 \text{ V} - (17 \text{ mA})(560 \Omega) = 2.48 \text{ V}$

$$\begin{aligned} \text{\%age change in } I_C &= \frac{I_C(75^\circ\text{C}) - I_C(25^\circ\text{C})}{I_C(25^\circ\text{C})} \times 100 \\ &= \frac{17 \text{ mA} - 11.3 \text{ mA}}{11.3 \text{ mA}} \times 100 = \mathbf{50\% \text{ (increase)}} \end{aligned}$$

Note that I_C changes by the same percentage as β .

$$\begin{aligned} \text{\%age change in } V_{CE} &= \frac{V_{CE}(75^\circ\text{C}) - V_{CE}(25^\circ\text{C})}{V_{CE}(25^\circ\text{C})} \times 100 \\ &= \frac{2.48 \text{ V} - 5.67 \text{ V}}{5.67 \text{ V}} \times 100 = \mathbf{-56.3\% \text{ (decrease)}} \end{aligned}$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

In addition to being affected by change in β , the Q-point is also affected by changes in V_{BE} and I_{CBO} in the base bias method.

(i) Effect of V_{BE} :

The base-emitter-voltage V_{BE} decreases with the increase in temperature (and vice-versa). The expression for I_B in base bias method is given by ;

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

It is clear that decrease in V_{BE} increases I_B . This will shift the Q-point ($I_C = \beta I_B$ and $V_{CE} = V_{CC} - I_C R_C$). The effect of change in V_{BE} is negligible if $V_{CC} \gg V_{BE}$ (V_{CC} atleast 10 times greater than V_{BE}).

(ii) Effect of I_{CBO} :

The reverse leakage current I_{CBO} has the effect of decreasing the net base current and thus increasing the base voltage. It is because the flow of I_{CBO} creates a voltage drop across R_B that adds to the base voltage as shown in Fig. 7. Therefore, change in I_{CBO} shifts the Q-point of the base bias circuit.

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

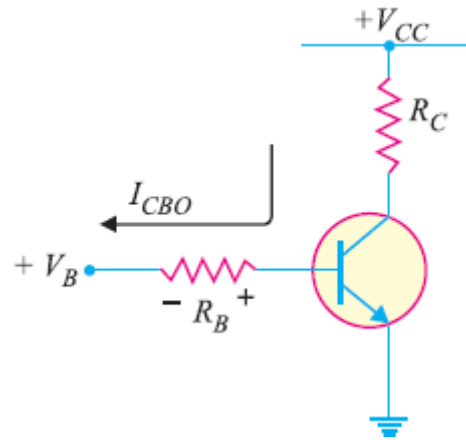


Fig. 7

However, in modern transistors, I_{CBO} is usually less than 100 nA and its effect on the bias is negligible if $V_{BB} \gg I_{CBO} R_B$.

Q10. Fig. 8 (i) shows the base resistor transistor circuit. The device (i.e. transistor) has the characteristics shown in Fig. 8 (ii). Determine V_{CC} , R_C and R_B .



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

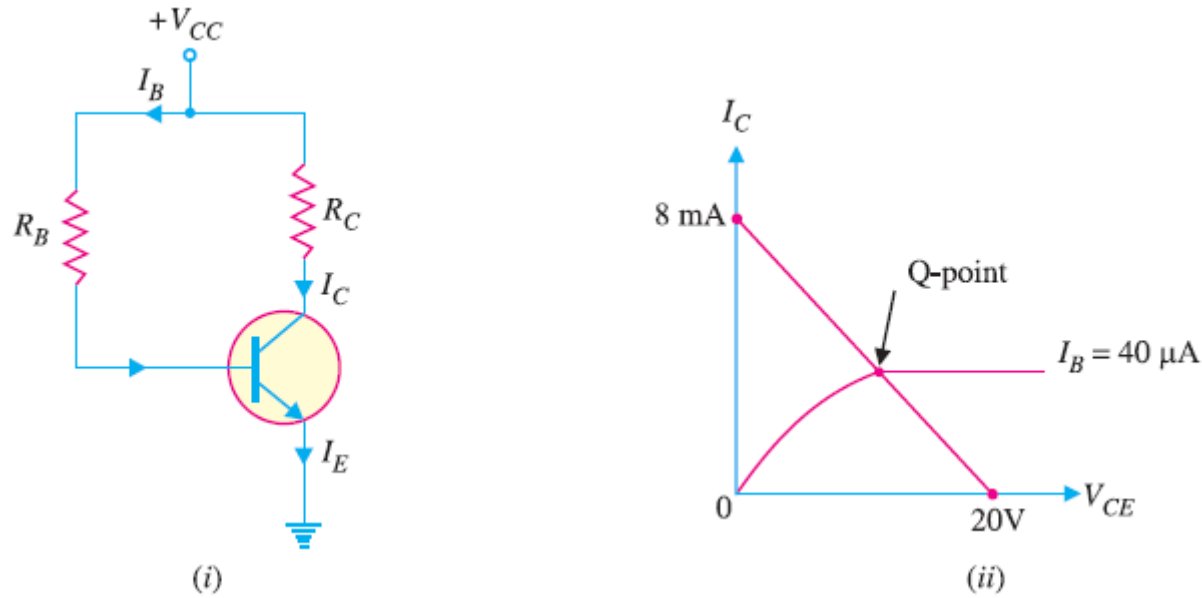


Fig. 8

Solution :

From the d.c load line, $V_{CC} = 20V$.

$$\text{Max. } I_C = \frac{V_{CC}}{R_C} \text{ (when } V_{CE} = 0V)$$

$$\therefore R_C = \frac{V_{CC}}{\text{Max. } I_C} = \frac{20V}{8mA} = 2.5 \text{ k}\Omega$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Q11. What fault is indicated in (i) Fig. 9 (i) and (ii) Fig. 9 (ii) ?

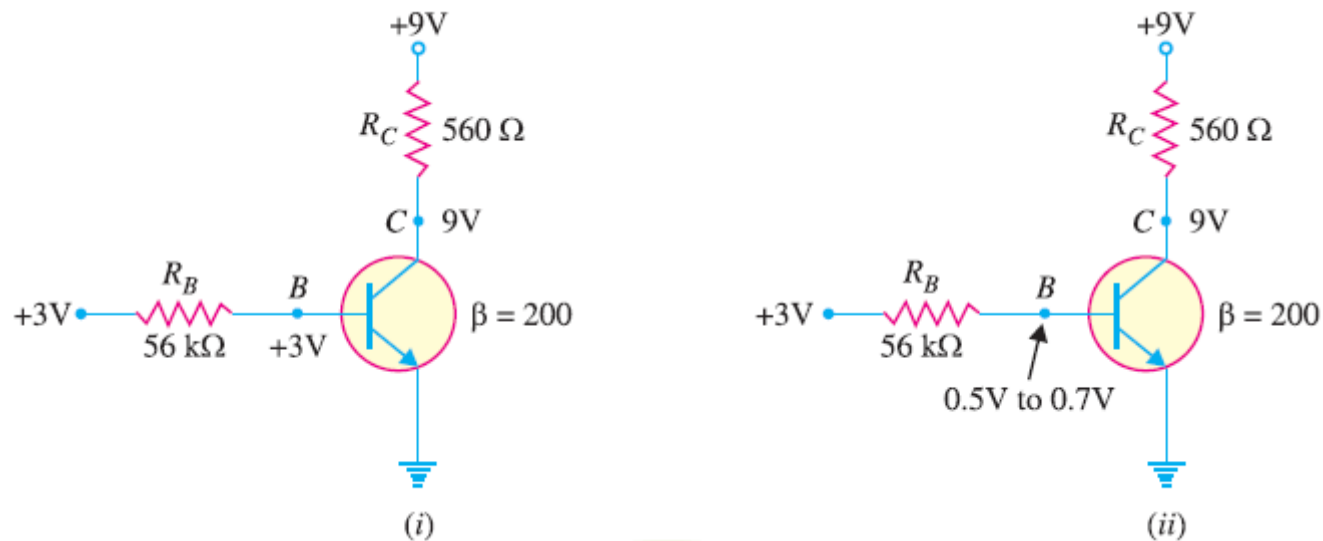


Fig. 9

Solution :

(i) The obvious fault in Fig. 9(i) is that the **base is internally open**. It is because 3V at the base and 9V at the collector mean that transistor is in cut-off state.

(ii) The obvious fault in Fig. 9 (ii) is that **collector is internally open**. The voltage at the base is correct. The voltage of 9V appears at the collector because the

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Q12. For the emitter bias circuit shown in Fig. 10, find I_E , I_C , V_C and V_C and V_{CE} for $\beta = 85$ and $V_{BE} = 0.7V$.

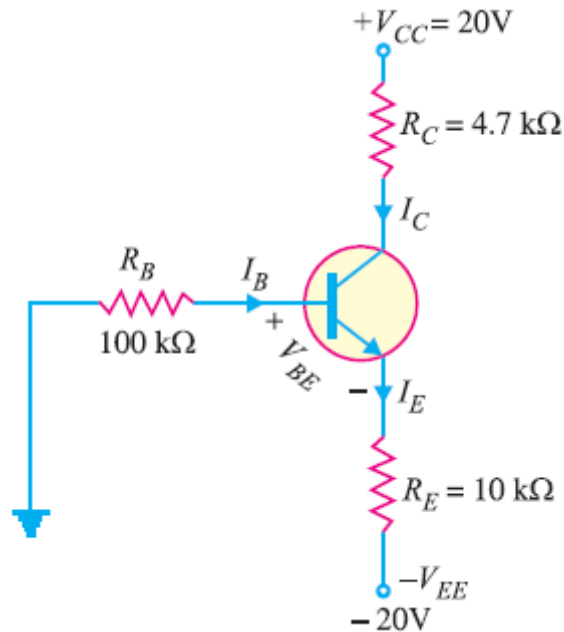


Fig. 10

Solution :

$$I_E \approx I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{20V - 0.7V}{10k\Omega} = 1.73mA$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Q13. Determine how much the Q-point in Fig. 11 will change over a temperature range where β increases from 85 to 100 and V_{BE} decreases from 0.7V to 0.6V.

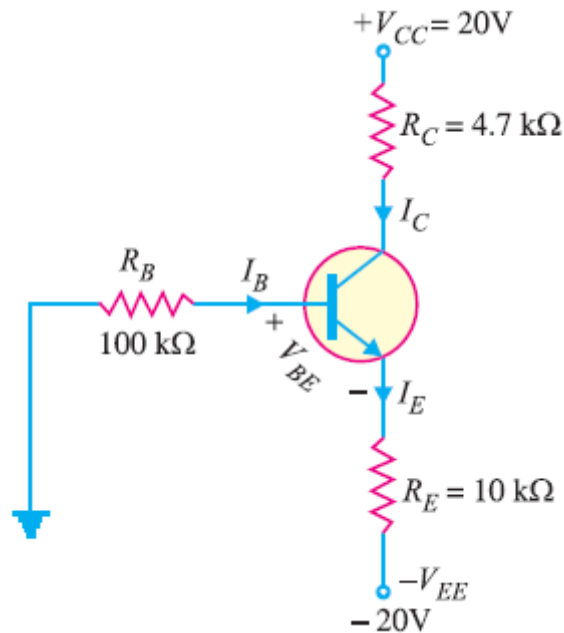


Fig. 11

Solution :

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

For $\beta = 100$ and $V_{BE} = 0.6V$

$$I_C \simeq I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B / \beta} = \frac{20V - 0.6V}{10 \text{ k}\Omega + 100 \text{ k}\Omega / 100} = \frac{19.4V}{11 \text{ k}\Omega} = 1.76 \text{ mA}$$

$$V_C = V_{CC} - I_C R_C = 20V - (1.76 \text{ mA}) (4.7 \text{ k}\Omega) = 11.7V$$

$$V_E = -V_{EE} + I_E R_E = -20V + (1.76 \text{ mA}) (10 \text{ k}\Omega) = -2.4V$$

$$\therefore V_{CE} = V_C - V_E = 11.7 - (-2.4) = 14.1V$$

$$\% \text{ age change in } I_C = \frac{1.76 \text{ mA} - 1.73 \text{ mA}}{1.73 \text{ mA}} \times 100 = \mathbf{1.7\% \text{ (increase)}}$$

$$\% \text{ age change in } V_{CE} = \frac{14.1V - 14.6V}{14.1V} \times 100 = \mathbf{-3.5\% \text{ (decrease)}}$$

Q14. Fig. 12 shows a silicon transistor biased by collector feedback resistor method. Determine the operating point. Given that $\beta = 100$.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

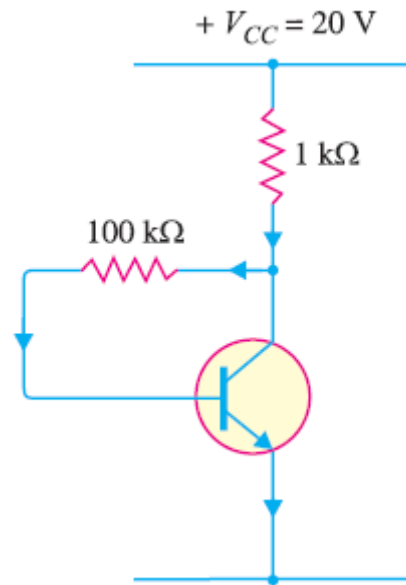


Fig. 12

Solution :

$V_{CC} = 20V$, $R_B = 100\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$

Since it is a silicon transistor, $V_{BE} = 0.7\text{ V}$.

Assuming I_B to be in mA and using the relation,



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$R_B = \frac{V_{CC} - V_{BE} - \beta I_B R_C}{I_B}$$

or $100 \times I_B = 20 - 0.7 - 100 \times I_B \times 1$

or $200 I_B = 19.3$

or $I_B = \frac{19.3}{200} = 0.096 \text{ mA}$

\therefore Collector current, $I_C = \beta I_B = 100 \times 0.096 = 9.6 \text{ mA}$

Collector-emitter voltage is

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 20 - 9.6 \text{ mA} \times 1 \text{ k}\Omega \\ &= 10.4 \text{ V} \end{aligned}$$

\therefore Operating point is **10.4 V, 9.6 mA.**

Q15. (i) It is required to set the operating point by biasing with collector feedback resistor at $I_C = 1 \text{ mA}$, $V_{CE} = 8 \text{ V}$. If $\beta = 100$, $V_{CC} = 12 \text{ V}$, $V_{BE} = 0.3 \text{ V}$, how will you do it ?
(ii) What will be the new operating point if $\beta = 50$, all other circuit values remaining the same ?

Solution :

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Now, collector load is

$$R_C = \frac{V_{CC} - V_{CE}}{I_C} = \frac{(12 - 8) \text{ V}}{1 \text{ mA}} = 4 \text{ k}\Omega$$

$$\text{Also } I_B = \frac{I_C}{\beta} = \frac{1 \text{ mA}}{100} = 0.01 \text{ mA}$$

$$\begin{aligned} \text{Using the relation, } R_B &= \frac{V_{CC} - V_{BE} - \beta I_B R_C}{I_B} \\ &= \frac{12 - 0.3 - 100 \times 0.01 \times 4}{0.01} = 770 \text{ k}\Omega \end{aligned}$$

(ii) Now $\beta = 50$, and other circuit values remain the same.

$$\therefore V_{CC} = V_{BE} + I_B R_B + \beta I_B R_C$$

$$\text{or } 12 = 0.3 + I_B (R_B + \beta R_C)$$

$$\text{or } 11.7 = I_B (770 + 50 \times 4)$$

$$\text{or } I_B = \frac{11.7 \text{ V}}{970 \text{ k}\Omega} = 0.012 \text{ mA}$$

$$\therefore \text{Collector current, } I_C = \beta I_B = 50 \times 0.012 = 0.6 \text{ mA}$$

$$\therefore \text{Collector-emitter voltage, } V_{CE} = V_{CC} - I_C R_C = 12 - 0.6 \text{ mA} \times 4 \text{ k}\Omega = 9.6 \text{ V}$$

✓ \therefore New operating point is **9.6 V, 0.6 mA**.

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

collector feedback resistor R_B . If $\beta = 100$, find the value of R_B .

Solution :

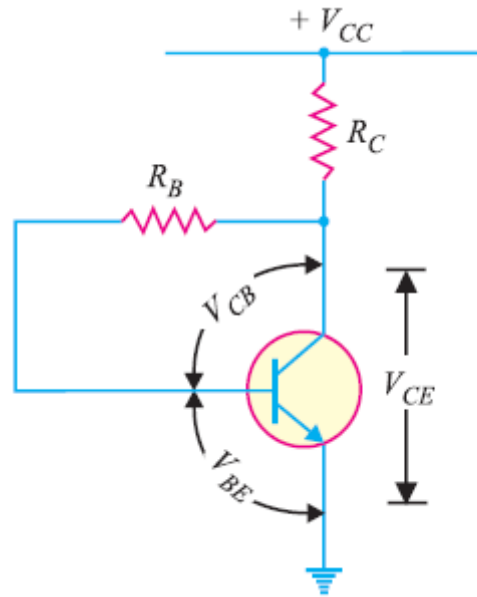


Fig. 13

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

For a silicon transistor,

$$V_{BE} = 0.7 \text{ V}$$

$$I_B = \frac{I_C}{\beta} = 1/100 = 0.01 \text{ mA}$$

Now $V_{CE} = V_{BE} + V_{CB}$

or $2 = 0.7 + V_{CB}$

$\therefore V_{CB} = 2 - 0.7 = 1.3 \text{ V}$

$\therefore R_B = \frac{V_{CB}}{I_B} = \frac{1.3\text{V}}{0.01 \text{ mA}} = 130 \text{ k}\Omega$

Q17. Find the Q-point values (I_C and V_{CE}) for the collector feedback bias circuit shown in Fig. 14.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

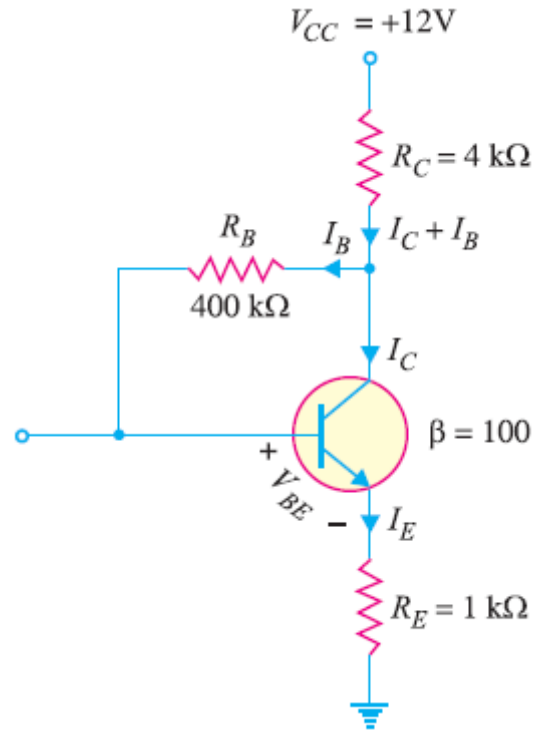


Fig. 14

Solution :

Fig. 14 shows the currents in the three resistors (R_C , R_B and R_E) in the circuit. By following the path through V_{CC} , R_C , R_B , V_{BE} and R_E and applying Kirchhoff's voltage law, we have,

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$\text{Now } I_B + I_C \simeq I_C; I_E \simeq I_C \text{ and } I_B = \frac{I_C}{\beta}$$

$$\therefore V_{CC} - I_C R_C - \frac{I_C}{\beta} R_B - V_{BE} - I_C R_E = 0$$

$$\text{or } I_C \left(R_E + \frac{R_B}{\beta} + R_C \right) = V_{CC} - V_{BE}$$

$$\therefore I_C = \frac{V_{CC} - V_{BE}}{R_E + R_B/\beta + R_C}$$

Putting the given circuit values, we have,

$$\begin{aligned} I_C &= \frac{12\text{V} - 0.7\text{V}}{1\text{ k}\Omega + 400\text{ k}\Omega/100 + 4\text{ k}\Omega} \\ &= \frac{11.3\text{V}}{9\text{ k}\Omega} = 1.26\text{ mA} \end{aligned}$$

$$\begin{aligned} V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 12\text{V} - 1.26\text{ mA} (4\text{k}\Omega + 1\text{ k}\Omega) \\ &= 12\text{V} - 6.3\text{V} = 5.7\text{V} \end{aligned}$$

\therefore The operating point is **5.7V, 1.26 mA**.

Q18. Find the d.c. bias values for the collector-feedback biasing circuit shown in Fig. 15. How does the circuit maintain a stable Q point against temperature variations ?

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

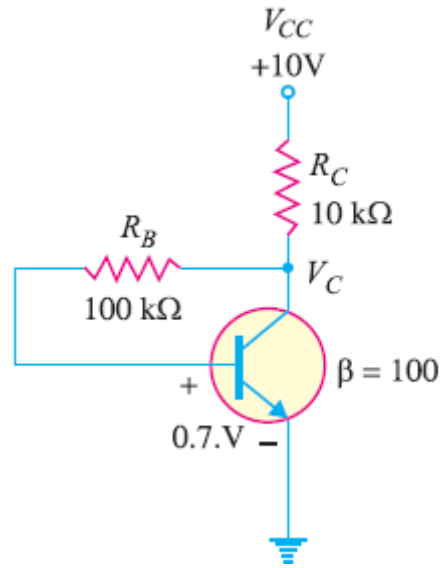


Fig.15

Solution :

The collector current is

$$\begin{aligned}
 I_C &= \frac{V_{CC} - V_{BE}}{R_E + R_B / \beta + R_C} \\
 &= \frac{10\text{V} - 0.7\text{V}}{0 + 100\text{ k}\Omega / 100 + 10\text{ k}\Omega} \\
 &= \frac{9.3\text{V}}{11\text{ k}\Omega} = 0.845\text{ mA}
 \end{aligned}$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Stability of Q-point :

We know that β varies directly with temperature and V_{BE} varies inversely with temperature. As the temperature goes up, β goes up and V_{BE} goes down. The increase in β increases $I_C (= \beta I_B)$. The decrease in V_{BE} increases I_B which in turn increases I_C . As I_C tries to increase, the voltage drop across $R_C (= I_C R_C)$ also tries to increase. This tends to reduce collector voltage V_C and, therefore, the voltage across R_B . The reduced voltage across R_B reduces I_B and offsets the attempted increase in I_C and attempted decrease in V_C . The result is that the collector feedback circuit maintains a stable Q-point. The reverse action occurs when the temperature decreases.

Q19. Fig. 16 shows the voltage divider bias method. Draw the d.c. load line and determine the operating point. Assume the transistor to be of silicon.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

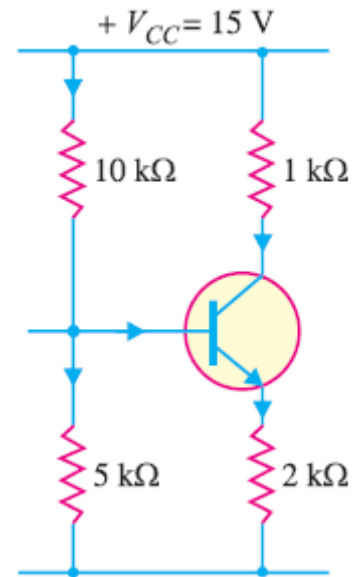


Fig. 16

Solution :

d.c. load line :

The collector-emitter voltage V_{CE} is given by :

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

When $I_C = 0$, $V_{CE} = V_{CC} = 15V$. This locates the first point B ($OB = 15V$) of the load line on the

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

This locates the second point A ($OA = 5 \text{ mA}$) of the load line on the collector current axis. By joining points A and B, the d.c. load line AB is constructed as shown in Fig. 17.

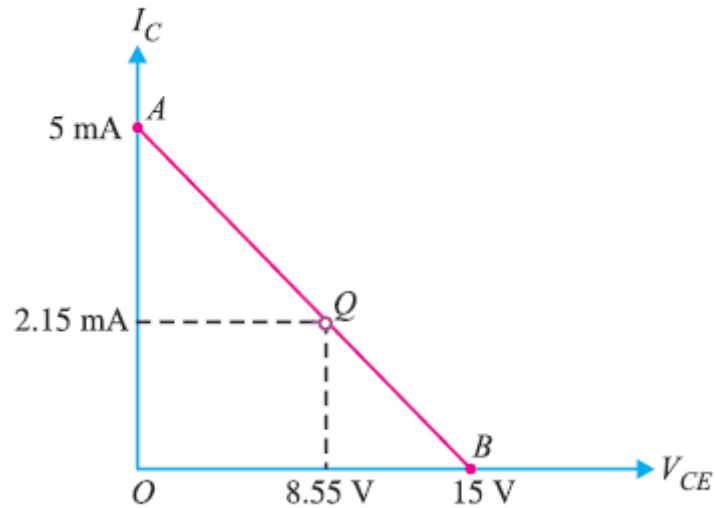


Fig. 17

Operating point :

For silicon transistor, $V_{BE} = 0.7 \text{ V}$



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Voltage across $5\text{ k}\Omega$ is

$$V_2 = \frac{V_{CC}}{10 + 5} \times 5 = \frac{15 \times 5}{10 + 5} = 5\text{ V}$$

$$\therefore \text{Emitter current, } I_E = \frac{V_2 - V_{BE}}{R_E} = \frac{5 - 0.7}{2\text{ k}\Omega} = \frac{4.3\text{ V}}{2\text{ k}\Omega} = 2.15\text{ mA}$$

\therefore Collector current is

$$I_C \simeq I_E = 2.15\text{ mA}$$

$$\begin{aligned} \text{Collector-emitter voltage, } V_{CE} &= V_{CC} - I_C(R_C + R_E) \\ &= 15 - 2.15\text{ mA} \times 3\text{ k}\Omega = 15 - 6.45 = 8.55\text{ V} \end{aligned}$$

\therefore Operating point is **8.55 V, 2.15 mA**.

Fig.17 shows the operating point Q on the load line. Its co-ordinates are $I_C = 2.15\text{ mA}$, $V_{CE} = 8.55\text{ V}$.

Q20. Calculate the emitter current in the voltage divider circuit shown in Fig. 18. Also find the value of VCE and collector potential VC.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

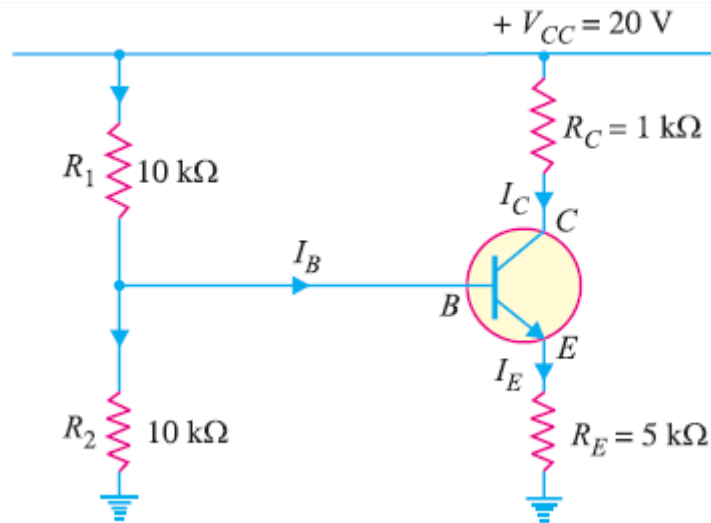


Fig. 18

Solution :

$$\text{Voltage across } R_2, V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) R_2 = \left(\frac{20}{10 + 10} \right) 10 = 10 \text{ V}$$

$$\text{Now } V_2 = V_{BE} + I_E R_E$$

As V_{BE} is generally small, therefore, it can be neglected.

$$\therefore I_E = \frac{V_2}{R_E} = \frac{10 \text{ V}}{5 \text{ k}\Omega} = 2 \text{ mA}$$

$$\text{Now } I_C \approx I_E = 2 \text{ mA}$$

$$\therefore V_{CE} = V_{CC} - I_C (R_C + R_E) = 20 - 2 \text{ mA} (6 \text{ k}\Omega)$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

Q21. For the circuit shown in Fig. 19, find the operating point. What is the stability factor of the circuit? Given that $\beta = 50$ and $V_{BE} = 0.7V$.

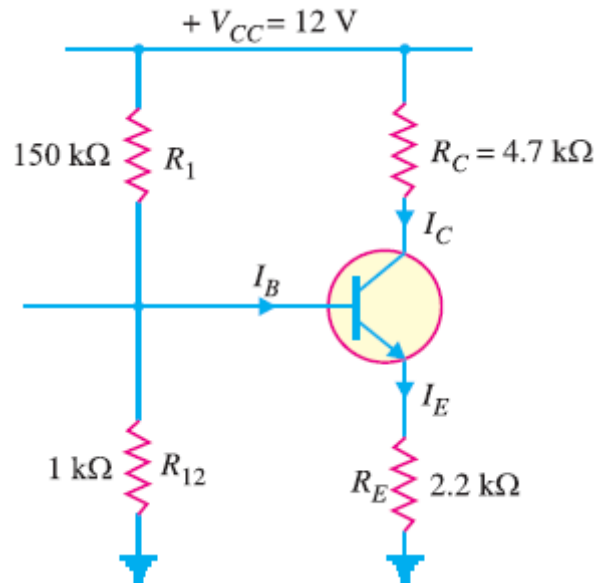


Fig. 19

Solution :

Fig. 19 shows the circuit of potential divider bias and Fig. 20 shows it with potential divider circuit replaced by Thevenin's equivalent circuit.

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

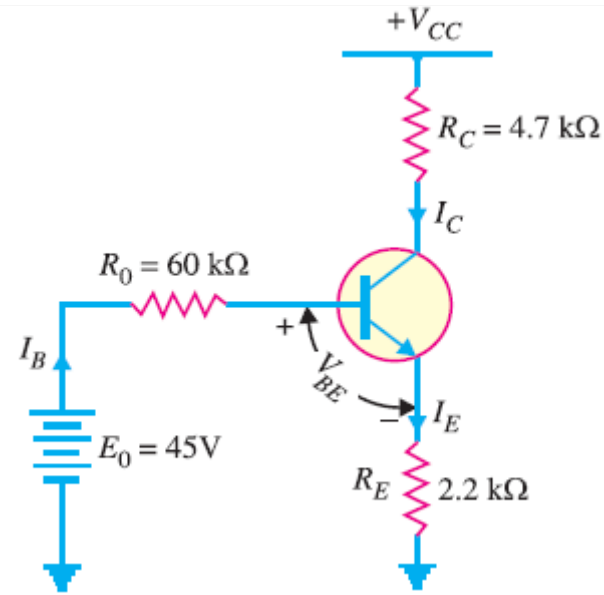


Fig. 20

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$E_0 = \frac{V_{CC}}{R_1 + R_2} \times R_2 = \frac{12V}{150 \text{ k}\Omega + 100 \text{ k}\Omega} \times 100 \text{ k}\Omega = 4.8V$$

$$R_0 = \frac{R_1 R_2}{R_1 + R_2} = \frac{150 \text{ k}\Omega \times 100 \text{ k}\Omega}{150 \text{ k}\Omega + 100 \text{ k}\Omega} = 60 \text{ k}\Omega$$

$$\begin{aligned} \therefore I_B &= \frac{E_0 - V_{BE}}{R_0 + \beta R_E} \quad \dots \\ &= \frac{4.8V - 0.7V}{60 \text{ k}\Omega + 50 \times 2.2 \text{ k}\Omega} = \frac{4.1V}{170 \text{ k}\Omega} = 0.024 \text{ mA} \end{aligned}$$

Now $I_C = \beta I_B = 50 \times 0.024 = 1.2 \text{ mA}$

$$\begin{aligned} \therefore V_{CE} &= V_{CC} - I_C (R_C + R_E) \\ &= 12V - 1.2\text{mA} (4.7 \text{ k}\Omega + 2.2 \text{ k}\Omega) = 3.72V \end{aligned}$$

\therefore Operating point is **3.72V, 1.2 mA**.

Now $\frac{R_0}{R_E} = \frac{60 \text{ k}\Omega}{2.2 \text{ k}\Omega} = 27.3$

$$\begin{aligned} \therefore \text{Stability factor, } S &= (\beta + 1) \times \frac{1 + R_0 / R_E}{\beta + 1 + R_0 / R_E} \\ &= (50 + 1) \times \frac{1 + 27.3}{50 + 1 + 27.3} = \mathbf{18.4} \end{aligned}$$

Q22. The circuit shown in Fig. 21 uses silicon transistor having $\beta = 100$. Find the operating point and stability factor.

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

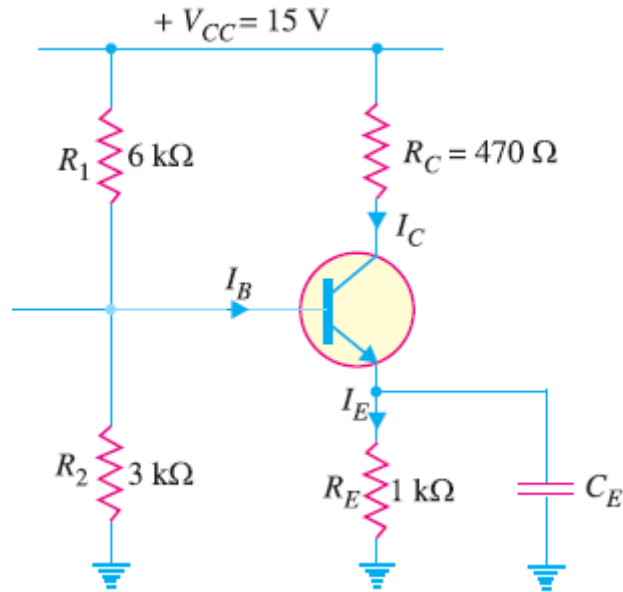


Fig. 21

Solution :

Fig. 21 shows the circuit of potential divider bias and Fig. 22 shows it with potential divider circuit replaced by Thevenin's equivalent circuit.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

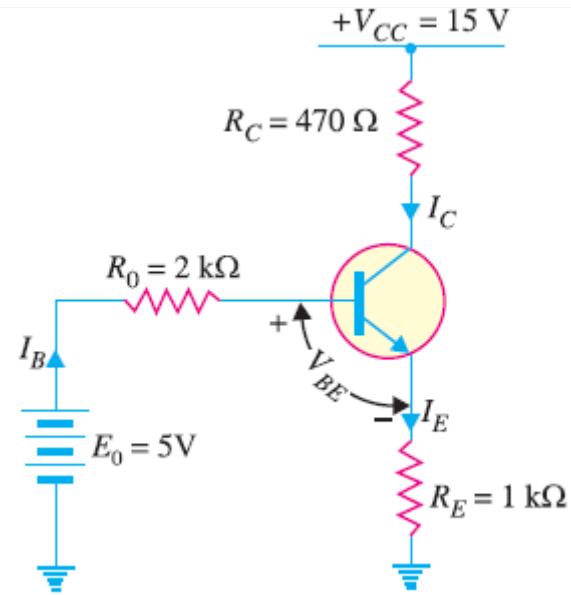


Fig. 22

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$E_0 = \frac{V_{CC}}{R_1 + R_2} \times R_2 = \frac{15V}{6 \text{ k}\Omega + 3 \text{ k}\Omega} \times 3 \text{ k}\Omega = \frac{15V}{9 \text{ k}\Omega} \times 3 \text{ k}\Omega = 5V$$

$$R_0 = \frac{R_1 R_2}{R_1 + R_2} = \frac{6 \text{ k}\Omega \times 3 \text{ k}\Omega}{6 \text{ k}\Omega + 3 \text{ k}\Omega} = 2 \text{ k}\Omega$$

Now

$$I_B = \frac{E_0 - V_{BE}}{R_0 + \beta R_E}$$

$$= \frac{5V - 0.7V}{2 \text{ k}\Omega + 100 \times 1 \text{ k}\Omega} = \frac{4.3V}{102 \text{ k}\Omega} = 0.042 \text{ mA}$$

$$\therefore I_C = \beta I_B = 100 \times 0.042 = 4.2 \text{ mA}$$

and

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

$$= 15V - 4.2 \text{ mA} (470\Omega + 1 \text{ k}\Omega) = 8.83V$$

\therefore Operating point is **8.83V ; 4.2 mA**.

Now $R_0/R_E = 2 \text{ k}\Omega / 1 \text{ k}\Omega = 2$

$$\therefore \text{Stability factor, } S = (\beta + 1) \times \frac{1 + R_0/R_E}{\beta + 1 + R_0/R_E}$$

$$= (100 + 1) \times \frac{1 + 2}{100 + 1 + 2} = \mathbf{2.94}$$

Q23. In the circuit shown in Fig. 23, the operating point is chosen such that $I_C = 2 \text{ mA}$, $V_{CE} = 3V$. If $R_C = 2.2 \text{ k}\Omega$, $V_{CC} = 9V$ and $\beta = 50$, determine the values of R_1 , R_2 and R_E . Take

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

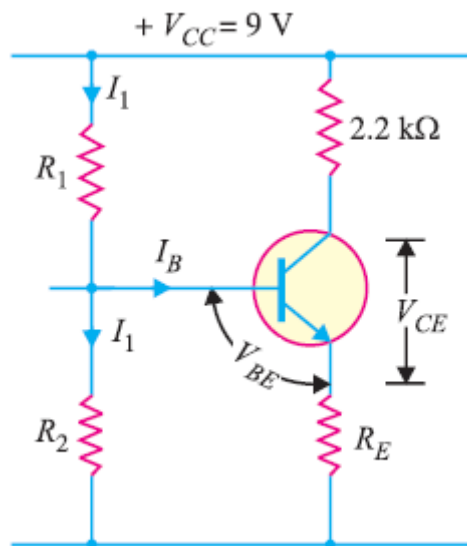


Fig. 23

Solution :

Given, $R_C = 2.2 \text{ k}\Omega$, $V_{CC} = 9\text{V}$ and $\beta = 50$, $V_{BE} = 0.3\text{V}$ and $I_1 = 10I_B$.

As I_B is very small as compared to I_1 , therefore, we can assume with reasonable accuracy that I_1 flowing through R_1 also flows through R_2 .



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$\text{Base current, } I_B = \frac{I_C}{\beta} = \frac{2 \text{ mA}}{50} = 0.04 \text{ mA}$$

Current through R_1 & R_2 is

$$I_1 = 10 I_B = 10 \times 0.04 = 0.4 \text{ mA}$$

$$\text{Now } I_1 = \frac{V_{CC}}{R_1 + R_2}$$

$$\therefore R_1 + R_2 = \frac{V_{CC}}{I_1} = \frac{9 \text{ V}}{0.4 \text{ mA}} = 22.5 \text{ k}\Omega$$

Applying Kirchhoff's voltage law to the collector side of the circuit, we get,

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E$$

$$\text{or } V_{CC} = I_C R_C + V_{CE} + I_C R_E \quad (\because I_C \approx I_E)$$

$$\text{or } 9 = 2 \text{ mA} \times 2.2 \text{ k}\Omega + 3 + 2 \text{ mA} \times R_E$$

$$\therefore R_E = \frac{9 - 4.4 - 3}{2} = 0.8 \text{ k}\Omega = \mathbf{800 \Omega}$$

$$\begin{aligned} \text{Voltage across } R_2, V_2 &= V_{BE} + V_E = 0.3 + 2 \text{ mA} \times 0.8 \text{ k}\Omega \\ &= 0.3 + 1.6 = 1.9 \text{ V} \end{aligned}$$

$$\therefore \text{Resistance } R_2 = V_2 / I_1 = 1.9 \text{ V} / 0.4 \text{ mA} = \mathbf{4.75 \text{ k}\Omega}$$

HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

calculate R_1 and R_C to place Q point at $I_C = 2\text{mA}$, $V_{CE} = 6\text{ volts}$.

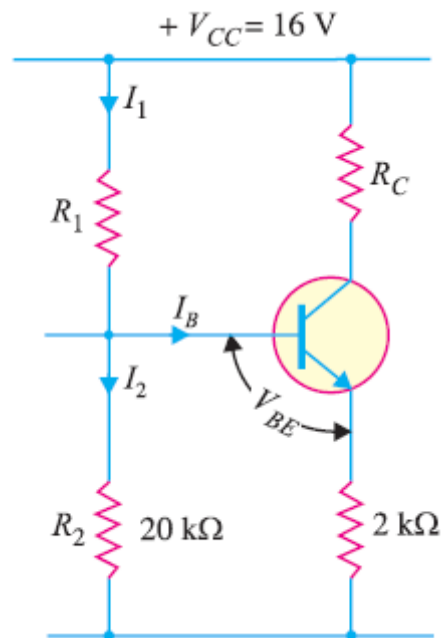


Fig. 24

Solution :

Given, $\alpha = 0.985$, $V_{BE} = 0.3\text{V}$ and $V_{CC} = 16\text{V}$



HV vacuum circuit breaker - 24KV vacuum
circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.985}{1 - 0.985} = 66$$

$$\text{Base current, } I_B = \frac{I_C}{\beta} = \frac{2 \text{ mA}}{66} = 0.03 \text{ mA}$$

$$\begin{aligned} \text{Voltage across } R_2, V_2 &= V_{BE} + V_E = 0.3 + 2 \text{ mA} \times 2 \text{ k}\Omega \\ &= 4.3 \text{ V} \end{aligned}$$

$$\therefore \text{ Voltage across } R_1 = V_{CC} - V_2 = 16 - 4.3 = 11.7 \text{ V}$$

\therefore Current through R_1 & R_2 is

$$I_1 = \frac{V_2}{R_2} = \frac{4.3 \text{ V}}{20 \text{ k}\Omega} = 0.215 \text{ mA}$$

$$\begin{aligned} \therefore \text{ Resistance } R_1 &= \frac{\text{Voltage across } R_1}{I_1} = \frac{11.7 \text{ V}}{0.215 \text{ mA}} \\ &= \mathbf{54.4 \text{ k}\Omega} \end{aligned}$$

$$\begin{aligned} \text{Voltage across } R_C &= V_{CC} - V_{CE} - V_E \\ &= 16 - 6 - 2 \times 2 = 6 \text{ V} \end{aligned}$$

$$\therefore \text{ Collector resistance, } R_C = \frac{\text{Voltage across } R_C}{I_C} = \frac{6 \text{ V}}{2 \text{ mA}} = \mathbf{3 \text{ k}\Omega}$$



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com



Hi! I am Sasmita . At ElectronicsPost.com I pursue my love for teaching. I am an M.Tech in Electronics & Telecommunication Engineering. And, if you really want to know more about me, please visit my "About" Page. [Read More](#)



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

- Sitemap
- Privacy Policy
- Terms of Use

- About
- Contact Us

- Basic Electronics Tutorials
- Communication Tutorials
- Basic Electronics Questions

Electronics Post Copyright © 2022.
ElectronicsPost.com is a participant in the Amazon Services LLC Associates Program, and we get a commission on purchases made through our links.



HV vacuum circuit breaker - 24KV vacuum circuit breaker

JGGY electrical provides high quality vacuum circuit breaker MV 12KV-40KV jggyelectrical.com

